

PAM

Components : Transistor BC547, signal generator, bread board, CRO

In a PAM communication system the continuous wave forms are sampled at continuous and regular intervals. They are transmitted along with the synchronising pulses. The original wave form can be constructed from the sample of receiving end if the sampled rate in any pulse modulation exceeds twice the maximum frequency. The original signal can be constructed in the receiver with minimal distortion.

The basic method for generation of PAM is that the signal to be modulated must be fed to a switch which is operated by sampling signal. It is the technique in which the analog signal is sampled and sampled value is used. There are two categories of pulse modulation. Digital pulse modulation and amplitude pulse modulation.

PAM is an analog pulse modulation in which the amplitude or a constant width and constant position pulse train is varied according to amplitude of analog signal. The process is termed as sampling of analog signal. There must be followed the sampling theorem.... that is if the sampling rate in any pulse modulation system exceeds twice the maximum signal frequency. The original signal can be constructed in receiver with minimal distortion.

PAM signals describe the time and value continuous. They are neither analog or digital. They are the intermediate stage of pulse code modulation.

Design

$V_{cc}: 5V$ $V_b: 5V$ $I_C: 2mA$ $\beta: 100$ $V_{be}: 0.7V$ $V_{ce}: sat: 0.2V$ $I_B: I_C/\beta = 20\mu A$ $I_B sat: 5 \times 20 = 100\mu A$

$R_c: (V_c - V_{ce sat})/I_C = (5 - 0.2)/2 \times 10^{-3} = 2.2k$ $R_b: V_b - V_{be}/I_B sat = 4.7k$

PWM

Components : 555ic, resistor, capacitor, DC power, Signal generator, CRO, bread board

For modulation of wave pulse modulation serves very well. In analog pulse modulation the indication of sample amplitude is variable. The continuous wave form is sampled at regular intervals information regarding the transmitted only at sampling times. Pulse width modulation is digital pulse modulation technique. In PWM the amplitude of starting time of all pulses are fixed in width of each pulse is made proportional to amplitude of signal at instant.

When the timer is connected at monostable mode and triggered with a continuous pulse train, the output width can be modulated by signal applied to Pin5 here the 555ic is used as a monostable multivibrator. When a trigger is applied to pin 2 the comparator switched the output to its unstable state. The unstable state is 1st position of flipflop. Now the capacitor charged and changes the flip flop output

to reset state by switching the output of comparator 1. The other output is $0.3/v_m$ when v_m is modulating signal. A negative going pulse of amplitude is greater than $1/3 v_m$ is needed as triggering signal. In the state the discharge transistor q_1 (inside 555) act as a short for the capacitor and in the two unstable state q_1 act as an open circuit to the external capacitor. The threshold voltage is given to non-inverting terminal of capacitor

Procedure: before feeding verify that 555 function as a stable multi vibrator by observing square wave on AF signal source. Keep it at 100Hz

Design. In monostable mode $T_{on} : 1.1 R C$ $T_{on} : 0.5 \text{ms}$ $C = 0.1 \mu\text{f}$

$$R = (0.5 - 10^{-3}) / (1.1 \times 0.1 \times 10^{-6}) = 4.7 \text{k ohm}$$

Frequency modulation

Components required : IC 565, resistor, capacitor, function generator, CRO, dc power, bread board

Modulation is the process by which information is encoded from a message source in order to optimize it for transmission. Frequency Modulation (FM) is the encoding of information in a carrier wave by changing the instantaneous frequency of the wave. FM technology is widely used in the fields of computing, telecommunications, and signal processing. Much like amplitude modulation, frequency modulation also has a similar approach, where a carrier signal is modulated by the input signal. However, in the case of FM, the amplitude of the modulated signal is kept, or it remains constant.

The frequency modulation index is mostly over 1, and it usually requires a high bandwidth at a range of 200 kHz. FM operates in a very high-frequency range, normally between 88 to 108 Megahertz. There are complex circuits with an infinite number of sidebands that help in receiving high-quality signals with high sound quality. Frequency modulation is widely used for FM radio broadcasting. It is also used in telemetry, radar, seismic prospecting, and monitoring newborns for seizures via EEG, [3] two-way radio systems, sound synthesis, magnetic tape-recording systems and some video-transmission systems. In radio transmission, an advantage of frequency modulation is that it has a larger signal-to-noise ratio and therefore rejects radio frequency interference better than an equal power amplitude modulation (AM) signal. For this reason, most music is broadcast over FM radio.

However, under severe enough multipath conditions it performs much more poorly than AM, with distinct high frequency noise artifacts that are audible with lower volumes and less complex tones. [citation needed] With high enough volume and carrier deviation audio distortion starts to occur that otherwise wouldn't be present without multipath or with an AM signal

Procedure : Feed 5Vpp and 1kHz square wave input

Set fm demodulator and

Design $V_{CC} : 5\text{V}$ at pin 16

Modulationn: R:10k ohm Input (pin9)at $v_{cc}/2=2.5v$

Message frequnecy1khz and amolitudd 1vpp R1=10k ohm (pin11)

R2=100 k ohm C=0.002mf